

# **INDUSTRIAL ELECTRONICS**

## **DDPE 3103**

### **TOPIC 3**

# **OSCILLATOR**

**PROF MADYA DR MORINA ABDULLAH | ENCIK KAMARUDDIN TAWI**  
**UTM KUALA LUMPUR CAMPUS**

# OSCILLATOR

- Oscillation is a form of **instability** caused by feedback that regenerates or reinforces a signal. The key to oscillator operation is **positive feedback**.
- Oscillators are circuits that **generates a periodic ac output** waveform **without an external** signal source (except DC supply).
- **Sinusoidal** oscillators produce a sine wave output while **multivibrators** produce square waves and rectangular pulses.

# The Barkhausen Criterion

In order for the system to oscillate, the circuit design must satisfy the **Barkhausen criterion**:

- **$A\beta = 1$**  (A is the amplitude gain and  $\beta$  is the feedback factor )
- **The total voltage phase shift** around the circuit loop is  $360^\circ$  or  $0^\circ$ .

# Types of Oscillator Circuits

1. Phase-Shift Oscillator
- 2. Wien Bridge Oscillator**
3. Tuned Oscillator Circuits
  - Colpitts
  - Hartley
- 4. Crystal Oscillators**

# 1. Phase - Shift Oscillator


The phase-shift oscillator uses the property of three RC filters to cause a phase shift of  $60^{\circ}$  degree each .

Frequency of the oscillator:

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

Feedback factor of the oscillator:


$$\beta = \frac{1}{29}$$

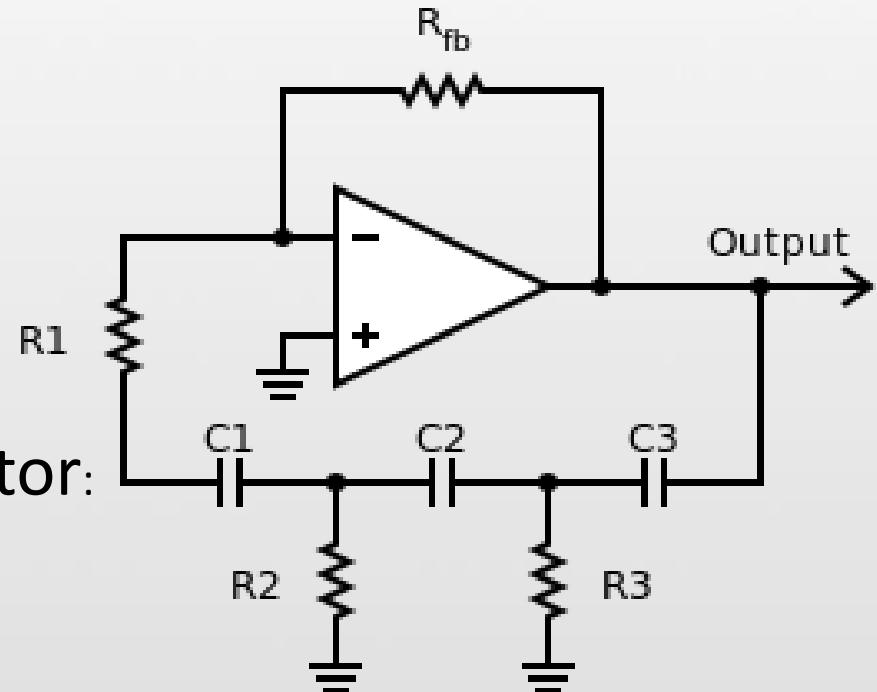
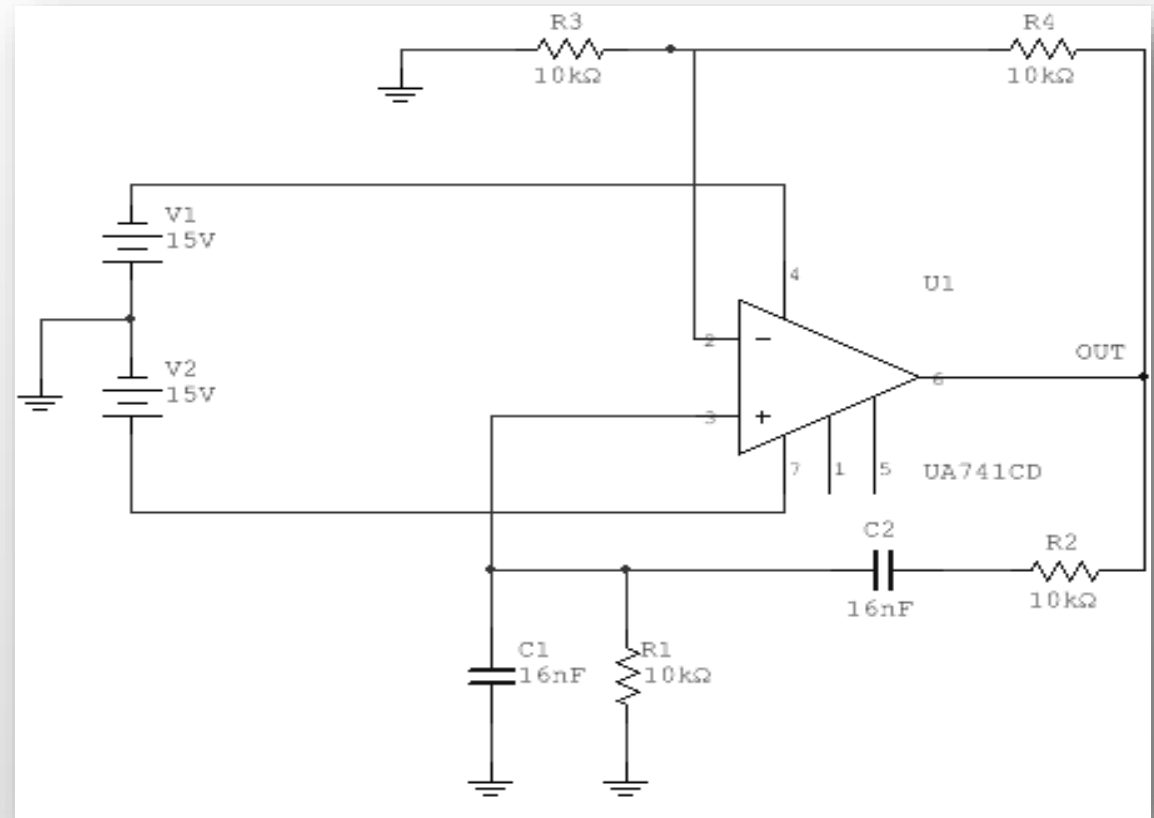
# Wien Bridge Oscillator

The Wien Bridge Oscillator can produce a large range of frequencies.

The Voltage gain of the amplifier must be greater than 3.




Frequency of oscillations:

$$f_o = \frac{1}{2\pi\sqrt{(R_1C_1R_2C_2)}}$$


# Tuned Oscillator Circuits

- i. The circuit consists of an **inductive coil, L** and a **capacitor, C**. The frequency of oscillations in the circuit depends upon the values of inductance of the coil and capacitance of the capacitor.
- ii. These oscillator are commonly used to produce **high range of frequencies** ranging from 1MHz to 500MHz and are also known as **radio frequencies (RF)**.
- iii. There are two common types:
  - **Colpitts**
    - The resonant circuit is an inductor and two capacitors.
  - **Hartley**
    - The resonant circuit is a tapped inductor or two inductors and one capacitor.
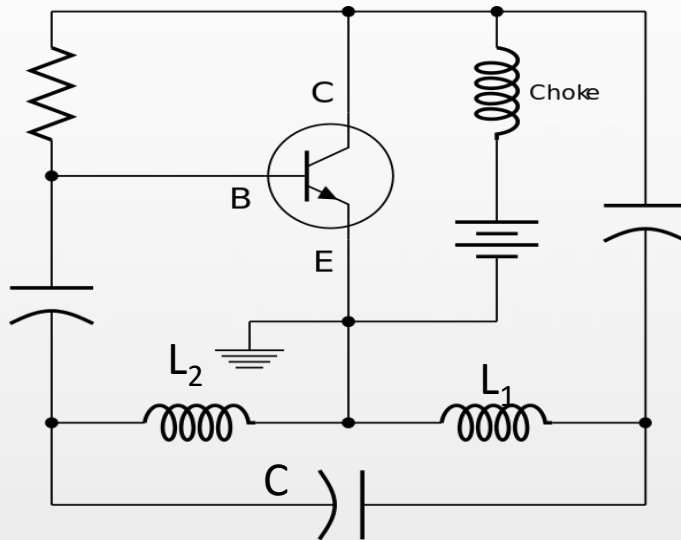
# Hartley Oscillator & Colpitts Oscillator



Hartley Oscillator

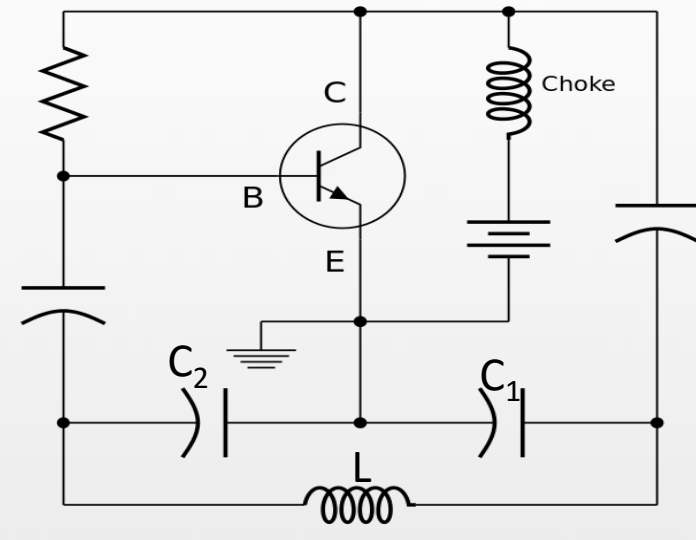

Colpitts Oscillator

Frequency of oscillations for Hartley oscillator :  $f_o = \frac{1}{2\pi\sqrt{(L_T C)}}$

Frequency of oscillations for Colpitts oscillator :  $f_o = \frac{1}{2\pi\sqrt{(LC_T)}}$



# CRYSTAL OSCILLATOR


- ❑ A **crystal oscillator** is an electronic **oscillator** circuit.
- ❑ The vibrating **crystal** of the piezoelectric material creates an electrical signal with a precise frequency.
- ❑ The purpose of the crystal oscillator is to produce **high frequency stability** of the output signal.


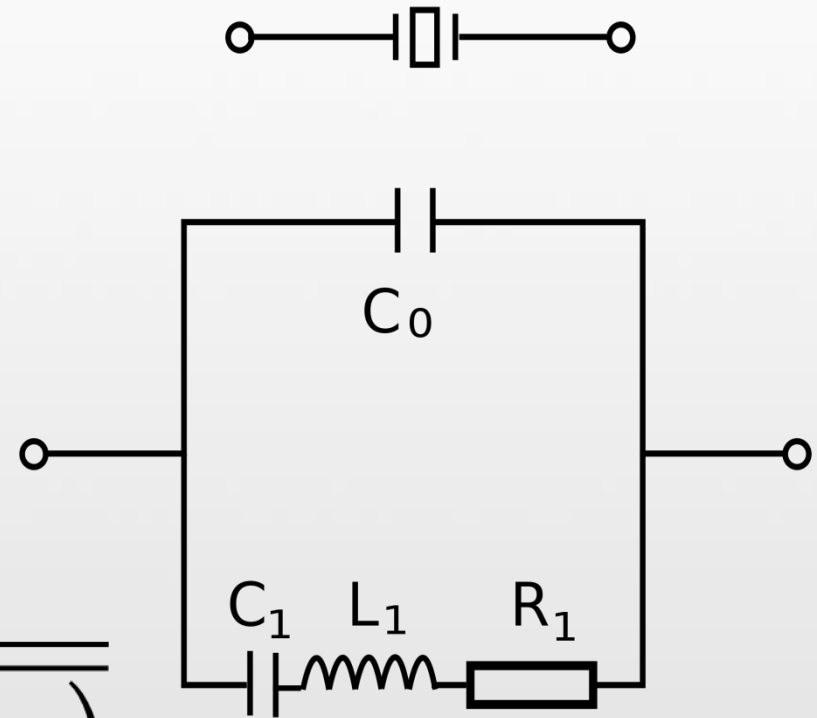
# Frequency Stability

$$f_{\text{series}} = \frac{1}{2\pi\sqrt{C_1 L_1}}$$

$$f_{\text{parallel}} = \frac{1}{2\pi\sqrt{L_1 \left( \frac{C_0 C_1}{C_0 + C_1} \right)}}$$




# MULTIVIBRATOR



- A multivibrator circuit **oscillates** between a “**HIGH**” state and a “**LOW**” state producing a continuous output which are square or rectangular waves.
- Types of multivibrator :
  - i. Astable**
    - A square wave oscillator.
  - ii. Bistable**
    - A digital device with two stable states.
  - iii. Monostable**
    - Has one stable state
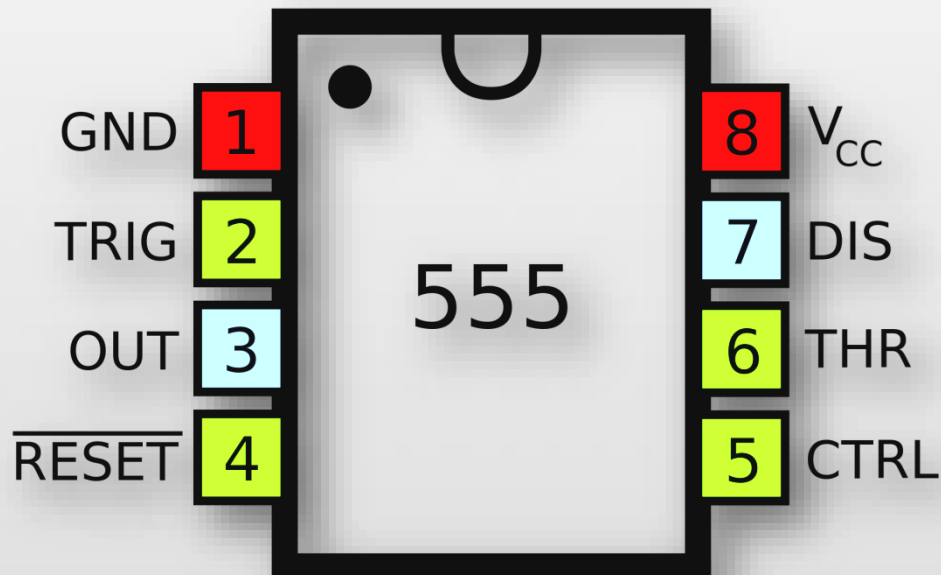
## 555 TIMER

- The most popular square wave oscillator is the 555 timer.



# ASTABLE MULTIVIBRATOR – TIMER 555

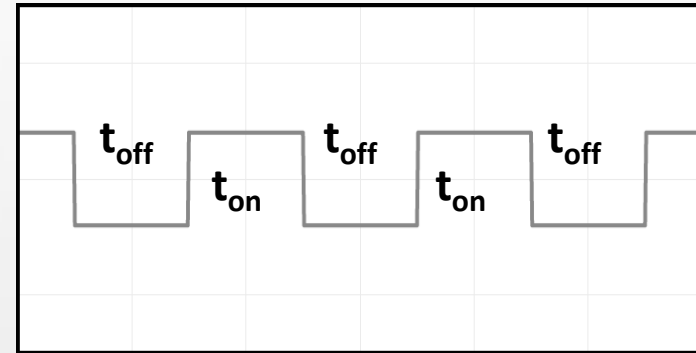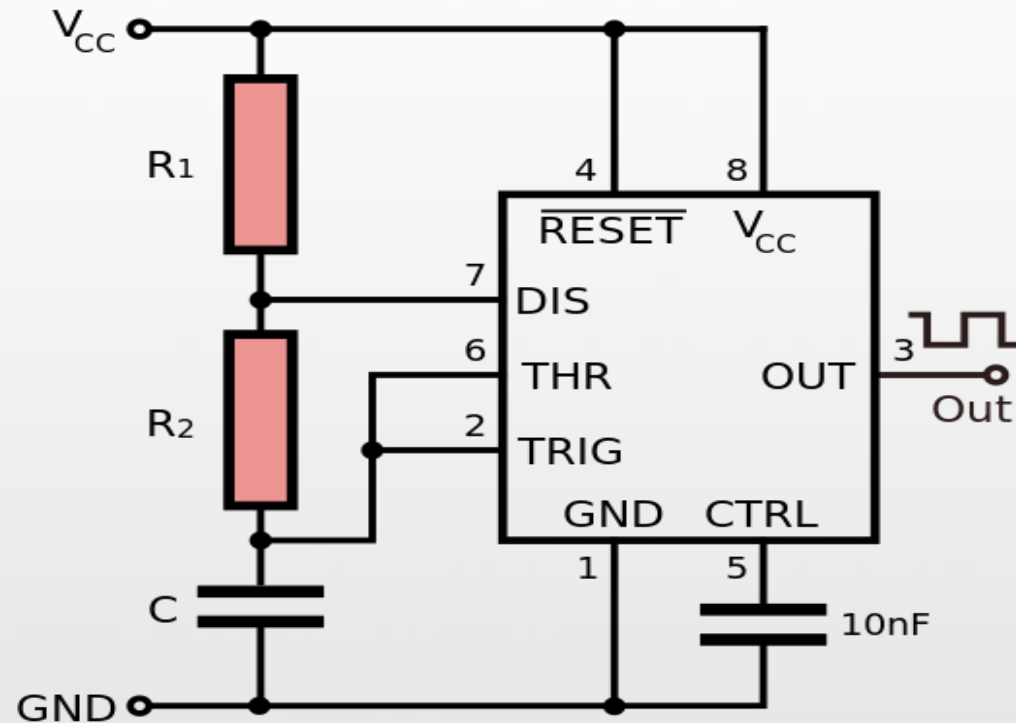

$$t_{on} = t_1$$


$$t_{off} = t_2$$

- $t_1 = 0.693 (R_1 + R_2) C$
- $t_2 = 0.693 R_2 C$
- $T = t_1 + t_2 = 0.693 (R_1 + 2R_2) C$
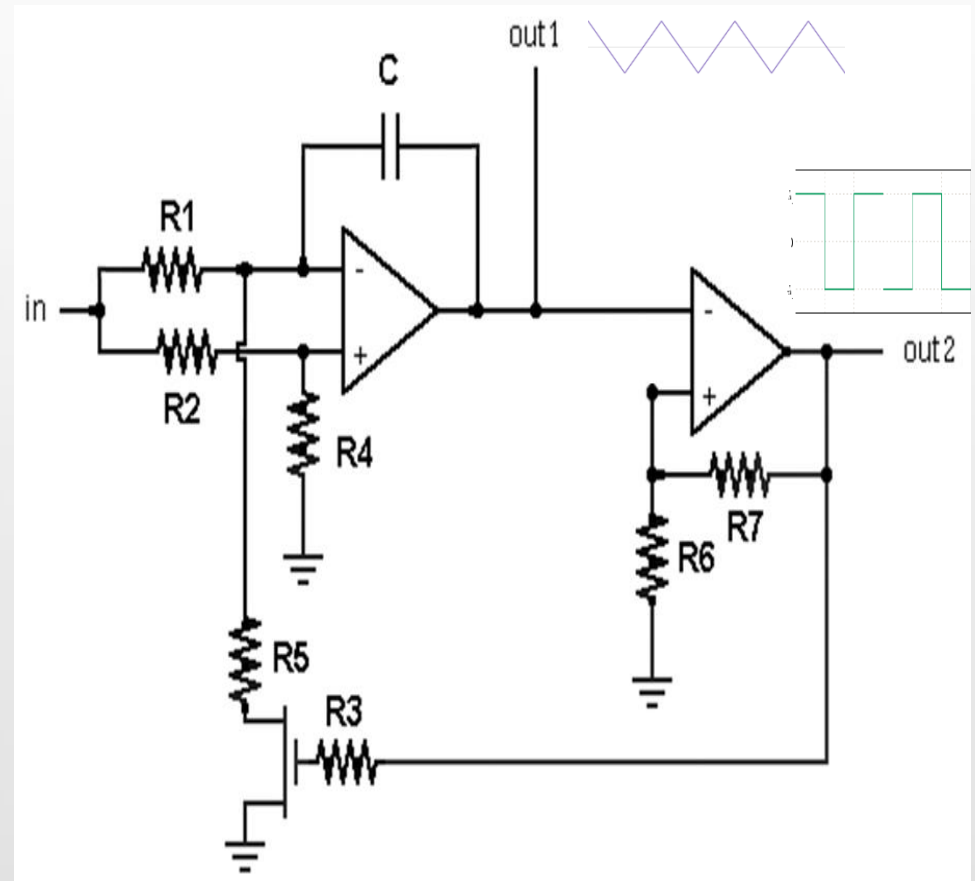
# Voltage Controlled Oscillator (VCO)

A VCO is a type of oscillator where the frequency of the output oscillations can be varied by varying the amplitude of an input voltage signal.

It consist of an **Integrator**, a **Schmitt trigger** and a **MOSFET**.



## References

1. Electronic Devices and Circuit Theory , Robert L. Boylestad & Louis Nashelsky , 9<sup>th</sup> Edition, 2006
2. Electronic Devices, Thomas L. Floyd, 5<sup>th</sup> Edition, 1999
3. Wikimedia Commons for images
4. Multisim Version 13.0