

SEE1223: Digital Electronics

2 – Logic Gates and Boolean Algebra

Zulkifil Md Yusof

Dept. of Microelectronics and Computer Engineering
The Faculty of Electrical Engineering
Universiti Teknologi Malaysia




Logic Gates and Boolean Algebra

- Logic Gates
 - Inverter, OR, AND, Buffer, NOR, NAND, XOR, XNOR
- Universal Gates
 - NAND and NOR
- Boolean Theorem
 - Commutative, Associative, Distributive
 - Basic Rules
- DeMorgan's Theorem
- Canonical/Standard Forms of Logic
 - Sum of Product (SOP)
 - Product of Sum (POS)
 - Minterm and Maxterm

Inverter/Not Gate

- Logic Symbol and Truth Table

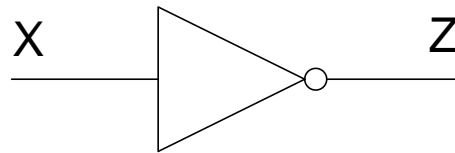

← Logic Symbol


Logic Expression

X	$Z = \overline{X}$
0	1
1	0

← Truth Table


Inverter/Not Gate

- Timing Diagram

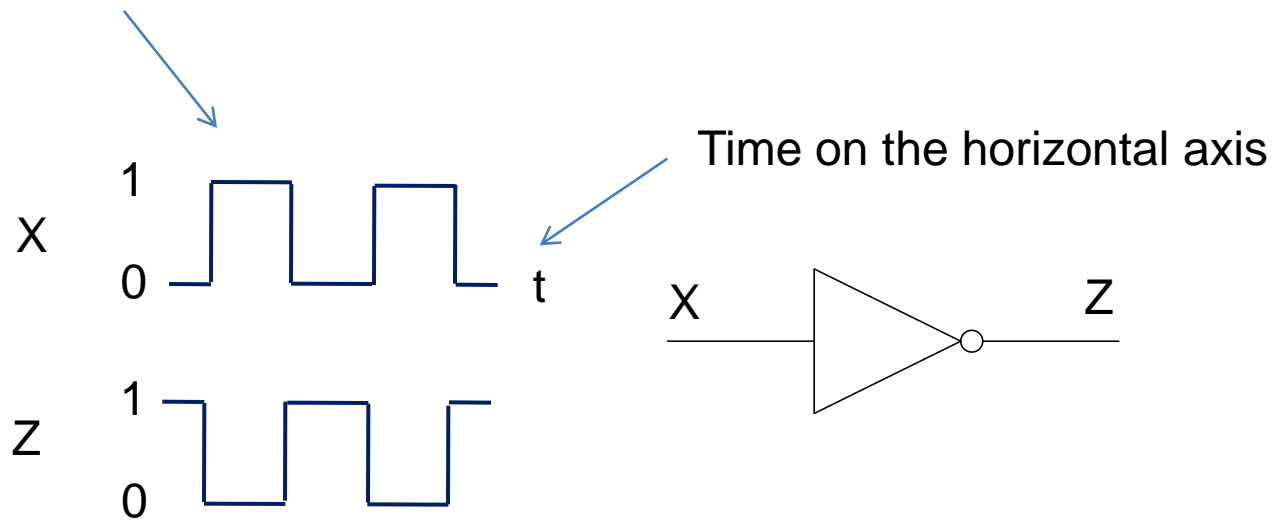

OR Gate


- Logic Symbol and Truth Table

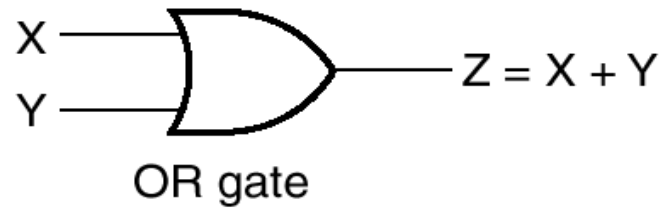

X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

AND Gate


- Logic Symbol and Truth Table

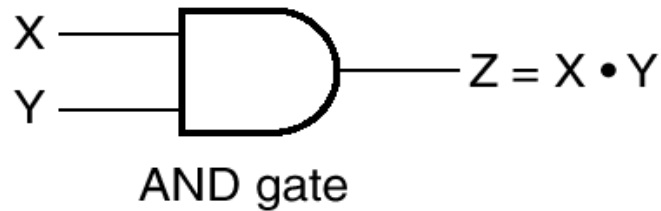

X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

Buffer


- Logic Symbol and Truth Table

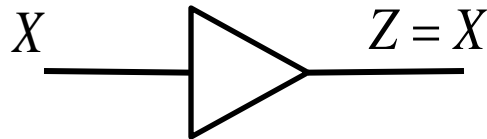

X	$Z = X$
0	0
1	1

Buffer


- How to design buffers? Clue: NOT gates

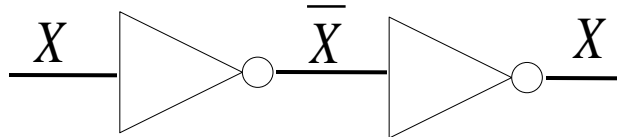

- What is the use of buffers?
 - Refresh weak signals
 - Purposely put delays

XOR

- Logic Symbol and Truth Table

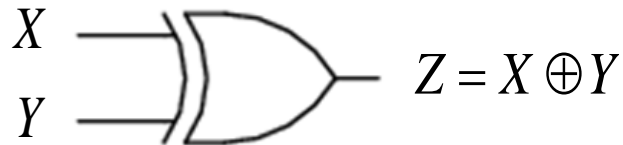


X	Y	$Z = X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

Result is '1' when exactly one input is '1'

XOR


- How to make XOR using basic gates (AND, OR, NOT)?
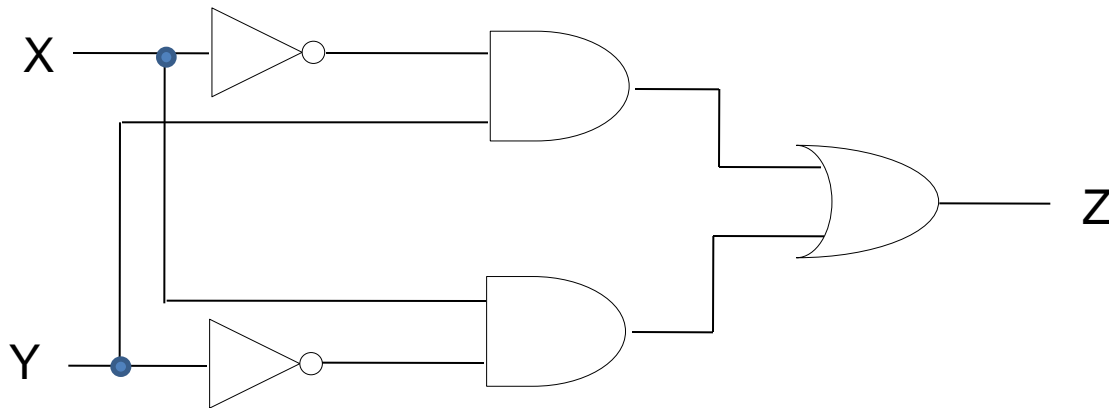
$$\begin{aligned} Z &= X \oplus Y \\ &= X \cdot \bar{Y} + \bar{X} \cdot Y \end{aligned}$$



XNOR

- Logic Symbol and Truth Table

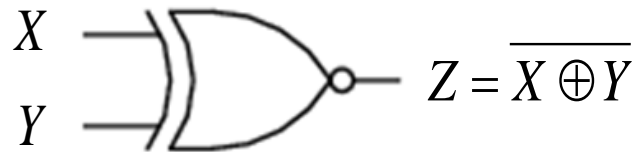


X	Y	$Z = \overline{X \oplus Y}$
0	0	1
0	1	0
1	0	0
1	1	1

Result is '1' when both inputs are the same logic

XNOR

- How to make XNOR using basic gates (AND, OR, NOT)?
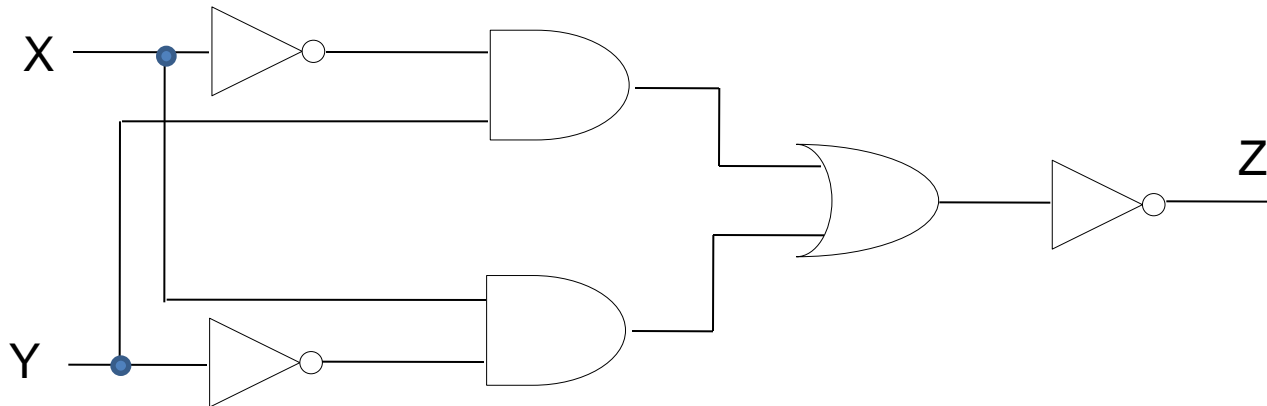
$$Z = \overline{X \oplus Y}$$
$$= \overline{X \cdot \bar{Y} + \bar{X} \cdot Y}$$



NOR

- Logic Symbol and Truth Table




X	Y	$Z = \overline{X + Y}$
0	0	1
0	1	0
1	0	0
1	1	0

Result is '1' only when both inputs are '0'

NOR


- How to make NOR gate using basic gates?

$$Z = \overline{X + Y}$$

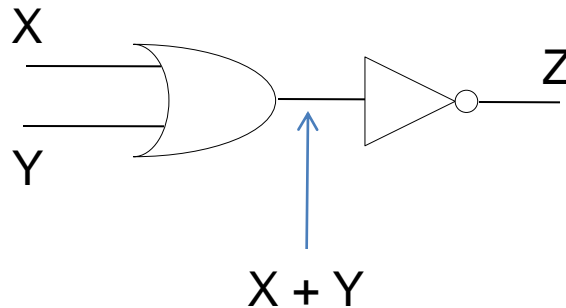

NAND

- Logic Symbol and Truth Table

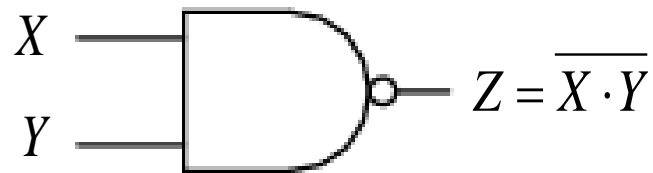


X	Y	$Z = \overline{X \cdot Y}$
0	0	1
0	1	1
1	0	1
1	1	0

Result is '0' only when both inputs are '1'

NAND

- How to make NAND gate using basic gates?

$$Z = \overline{X \cdot Y}$$

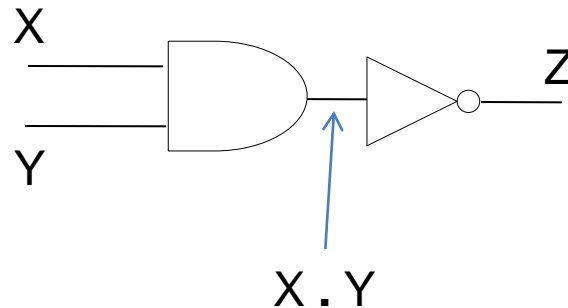

Example

- Draw the timing diagram for the following

