

Logic Gates and Boolean Algebra

- Logic Gates
 - Inverter, OR, AND, Buffer, NOR, NAND, XOR, XNOR
- Boolean Theorem
 - Commutative, Associative, Distributive Laws
 - Basic Rules
- DeMorgan's Theorem
- Universal Gates
 - NAND and NOR
- Canonical/Standard Forms of Logic
 - Sum of Product (SOP)
 - Product of Sum (POS)
 - Minterm and Maxterm

SOP and POS

- All boolean expressions can be converted to two standard forms:
 - SOP: Sum of Product
 - POS: Product of Sum
- Standardization of boolean expression makes evaluation, simplification, and implementation of boolean expressions more systematic and easier

Sum of Product (SOP)

- Boolean expressions are expressed as the sum of product, example:

$$ABC + CDE + \overline{BCD}$$

minterm

literal

- Each variable or their complements is called *literals*
- Each product term is called *minterm*

SOP (cont.)

- In SOP, a single overbar cannot extend over more than one variable, example:

$$AB + \overline{ABC} \leftarrow \text{Not SOP because } \overline{BC}$$

- Standard SOP* forms must contain all of the variables in the domain of the expression for each product term, example:

$$\overline{\overline{A}}\overline{\overline{B}}\overline{\overline{C}} + \overline{A}\overline{B}\overline{C} + ABC$$

SOP (cont.)

- In the following SOP form,

$$\overline{A}BC + \overline{A}\overline{B} + ABC\overline{D}$$

- How many minterms are there? $\Rightarrow 3$
- How many literals in the second product term? $\Rightarrow 2$
- Is it in a standard SOP form? \Rightarrow No
- How do we convert the boolean expression to standard SOP form?

SOP (cont.)

- To convert SOP to its standard form, we use the boolean rules

$$- A + \bar{A} = 1$$

$$- A(B + C) = AB + AC$$

- We have

$$\bar{A}\bar{B}C + \bar{A}\bar{B} + ABC\bar{D}$$

- The first product term is missing the variable D, and the second product term is missing C and D

SOP (cont.)

$$\overline{A}BC + \overline{A}\overline{B} + AB\overline{C}D$$

Apply $D + \overline{D} = 1$ and $C + \overline{C} = 1$

$$= \overline{A}BC(D + \overline{D}) + \overline{A}\overline{B}(C + \overline{C})(D + \overline{D}) + AB\overline{C}D$$

Apply the distributive law

$$= \overline{A}BCD + \overline{A}BC\overline{D} + (\overline{A}\overline{B}C + \overline{A}\overline{B}\overline{C})(D + \overline{D}) + AB\overline{C}D$$

$$= \overline{A}BCD + \overline{A}BC\overline{D} + \overline{A}\overline{B}CD + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} +$$

$$\overline{A}\overline{B}\overline{C}\overline{D} + AB\overline{C}D \quad \longleftarrow \quad \text{Standard SOP form}$$

Product of Sum (POS)

- Boolean expressions are expressed as the product of sum, example:

$$(\bar{A} + B)(A + \bar{B} + C)$$

literal

maxterm

POS (cont.)

- In POS, a single overbar cannot extend over more than one variable, example:

$$(\overline{A+B})(A+\overline{B+C}) \leftarrow \text{Not SOP because } \overline{B+C}$$

- Standard POS* forms must contain all of the variables in the domain of the expression for each sum term, example:

$$(A+B+C)(A+B+\overline{C})(A+\overline{B}+C)$$

POS (cont.)

- In the following POS form,

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

- Is it in a standard POS form? \Rightarrow No
- How do we convert the boolean expression to standard POS form?

POS (cont.)

- To convert POS to its standard form, we use the boolean rules

$$- A \cdot \bar{A} = 0$$

$$- A + BC = (A + B)(A + C)$$

- We have

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

- The first sum term is missing the variable D, and the second sum term is missing A

POS (cont.)

$$(A + \bar{B} + C)(\bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

Apply $D.\bar{D} = 0$ and $A.\bar{A} = 0$ to first and second terms

$$(A + \bar{B} + C + D.\bar{D})(A.\bar{A} + \bar{B} + C + \bar{D})(A + \bar{B} + \bar{C} + D)$$

Expand first and second terms

$$(A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})(A + \bar{B} + C + \bar{D})(\bar{A} + \bar{B} + C + \bar{D})$$

$$(A + \bar{B} + \bar{C} + D)$$

← Standard POS form

Minterm and Maxterm

- Minterm: Product terms in SOP
- Maxterm: Sum terms in POS
- Standard forms of SOP and POS can be derived from truth tables

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$A + B + C$$

$$\overline{A}\overline{B}C$$

$$A + \overline{B} + C$$

$$A + \overline{B} + \overline{C}$$

$$\overline{A} + B + C$$

$$\overline{A}BC$$

$$A\overline{B}\overline{C}$$

$$ABC$$

For SOP form,

$$Z = \overline{A}\overline{B}C + A\overline{B}\overline{C} + AB\overline{C} + ABC$$

$$= \sum m(1,5,6,7)$$

For POS form,

$$Z = (A + B + C)(A + \overline{B} + C)$$


$$(A + \overline{B} + \overline{C})(\overline{A} + B + C)$$

$$= \prod M(0,2,3,4)$$

Minterm and Maxterm

- How to design minterms – AND-OR logic
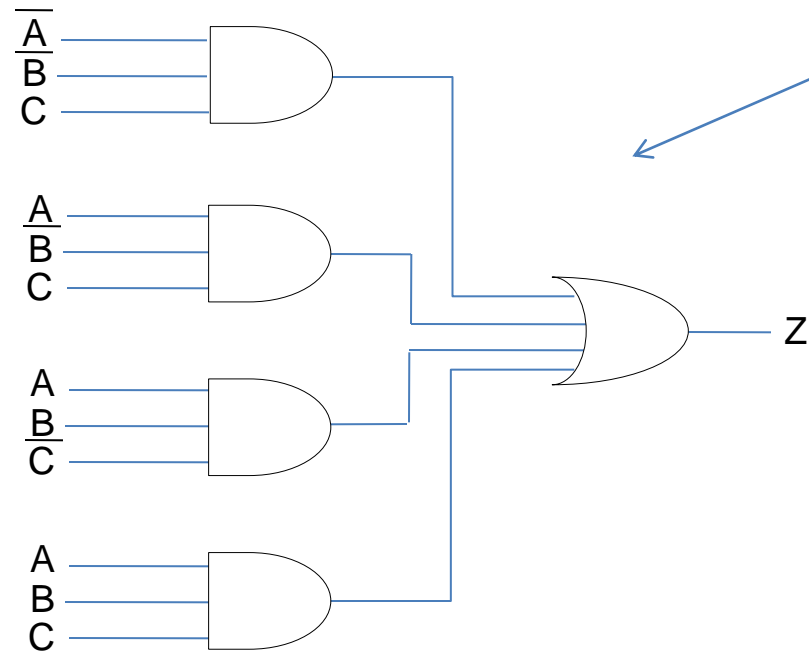
$$Z = \overline{\overline{A}}\overline{B}C + \overline{A}\overline{B}C + A\overline{B}C + ABC$$




Also known as
2 level logic

Minterm and Maxterm

- How to design minterms – NAND-NAND Logic
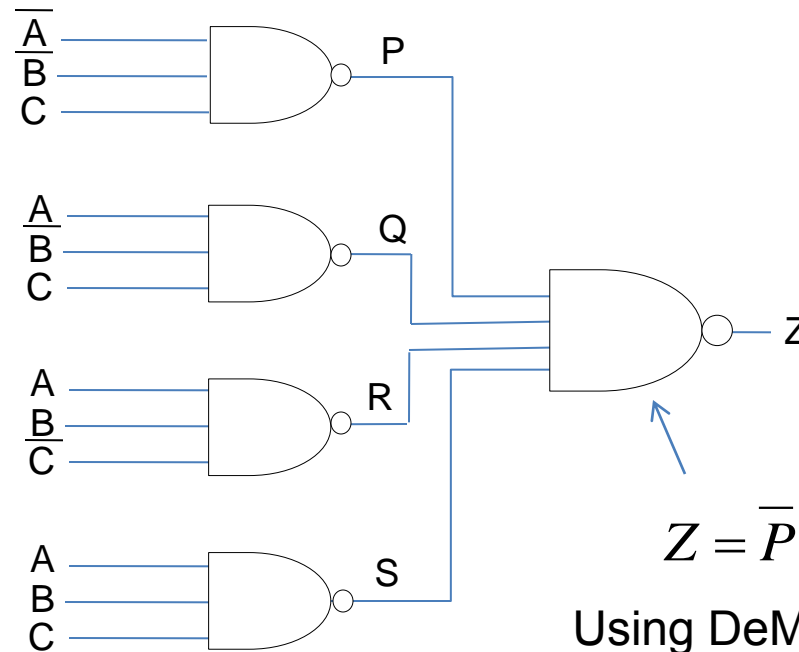
$$Z = \overline{\overline{A}}\overline{B}C + \overline{A}\overline{B}C + A\overline{B}C + ABC$$



$$Z = \overline{P} + \overline{Q} + \overline{R} + \overline{S}$$


Using DeMorgan's Theorem

$$Z = \overline{P \cdot Q \cdot R \cdot S}$$

Minterm and Maxterm

- How to design maxterms – OR-AND Logic

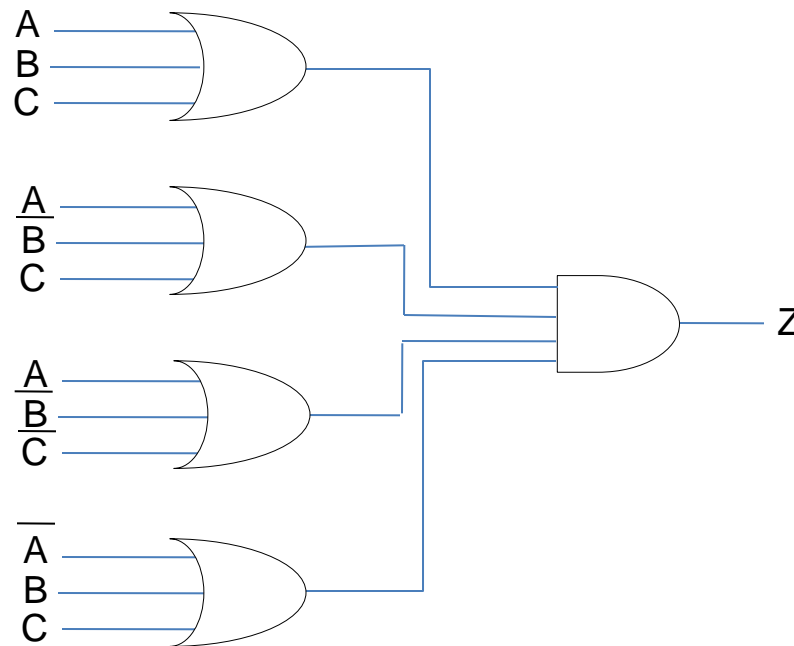
$$Z = (A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C)$$



Minterm and Maxterm

- How to design maxterms – NOR-NOR Logic
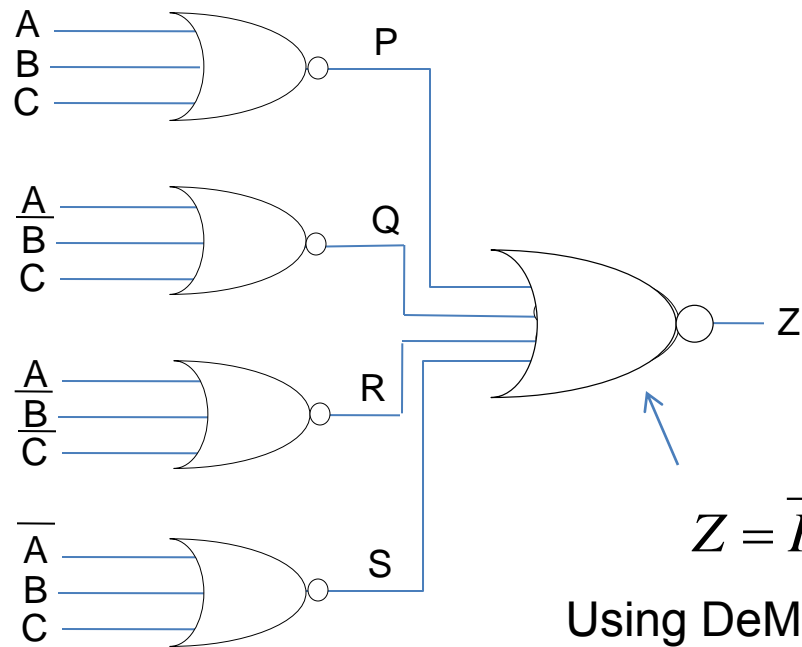
$$Z = (A + B + C)(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C)$$



$$Z = \overline{P + Q + R + S}$$

Minterm and Maxterm

- Can the minterm and maxterm logic be optimized?
 - Yes, using Boolean algebra – explore yourself
 - Yes, using Karnaugh maps – next lecture

